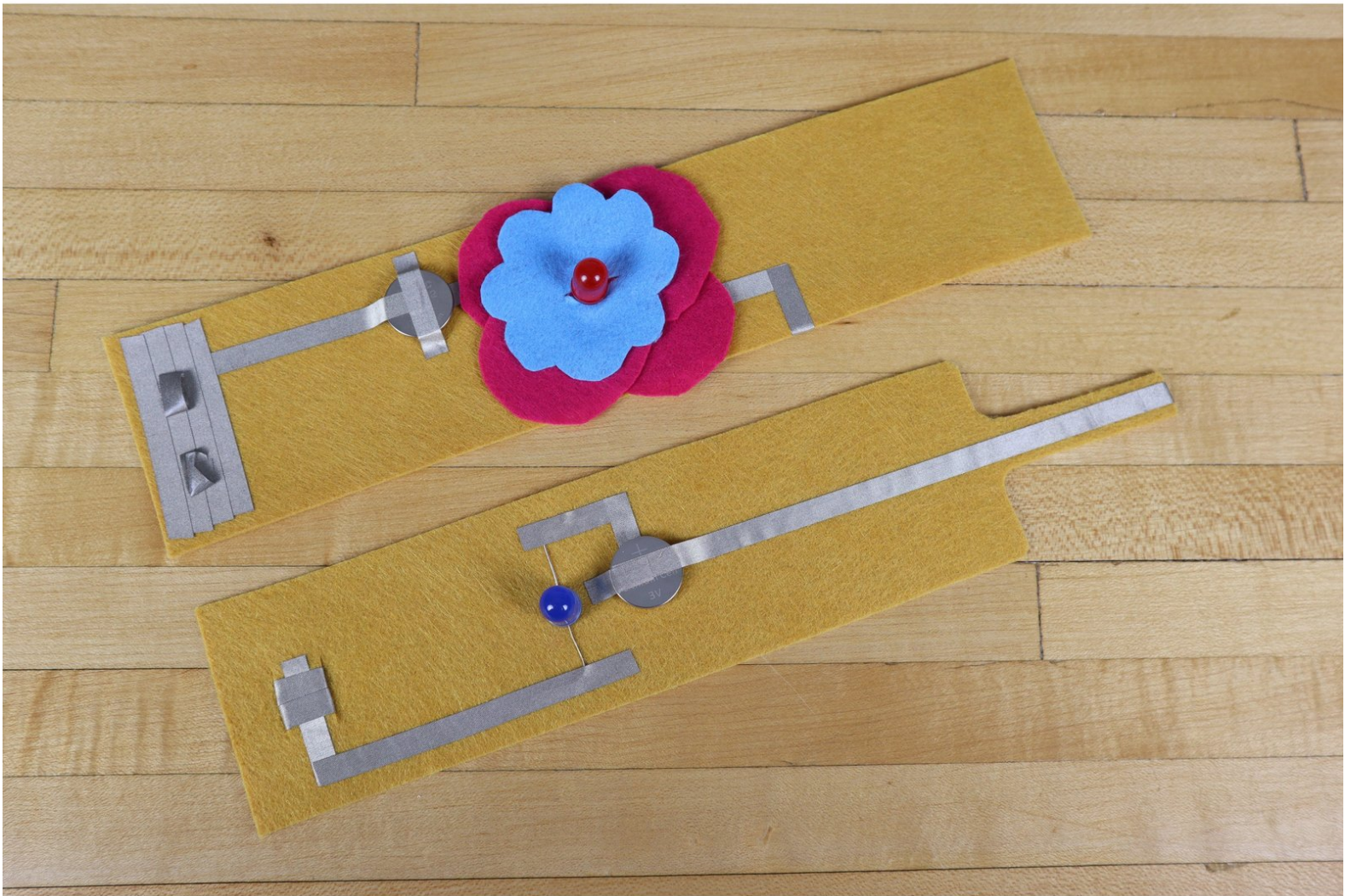




# No-Sew Conductive Bracelets

Make a No-Sew Conductive Bracelet using this guide. You'll need a battery, LED, and some Maker Tape™.

Written By: Pete Prodoehl



## INTRODUCTION

These bracelets can be made with paper or felt. Felt is a little more durable, though construction paper or cardstock can also be used.



### TOOLS:


- [Scissors](#) (1)



### PARTS:

- [Paper Circuits Kit](#) (1)

## Step 1 — No-Sew Conductive Bracelets

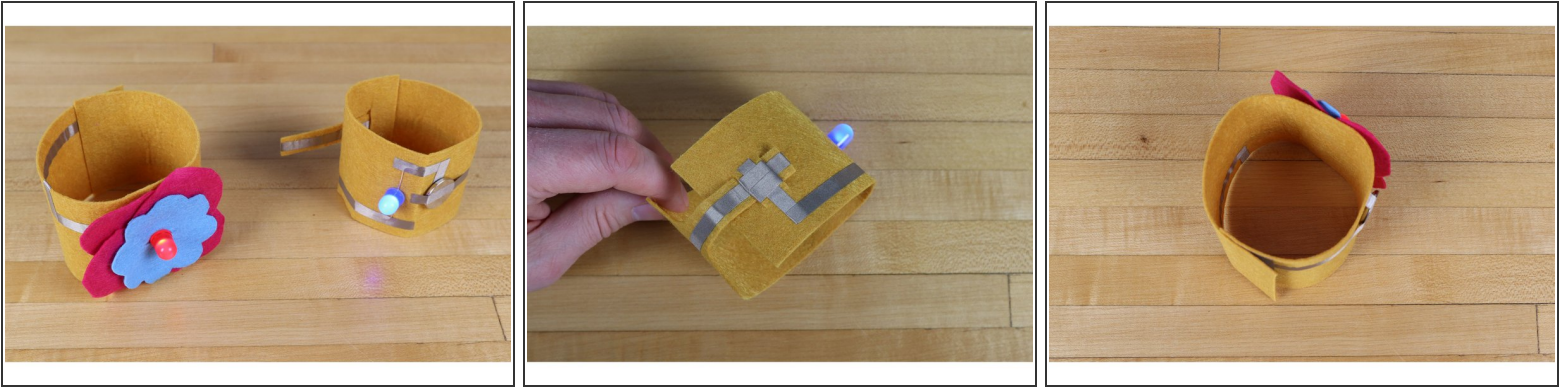

- Follow the guide to make your own no-sew conductive bracelet!
- When you connect the bracelet together, you complete the circuit to light up your LED.
- You can extend this project further by adding more LEDs or getting more decorative with the bracelet.
- Add a flower, a character, or other decorations to your bracelet.