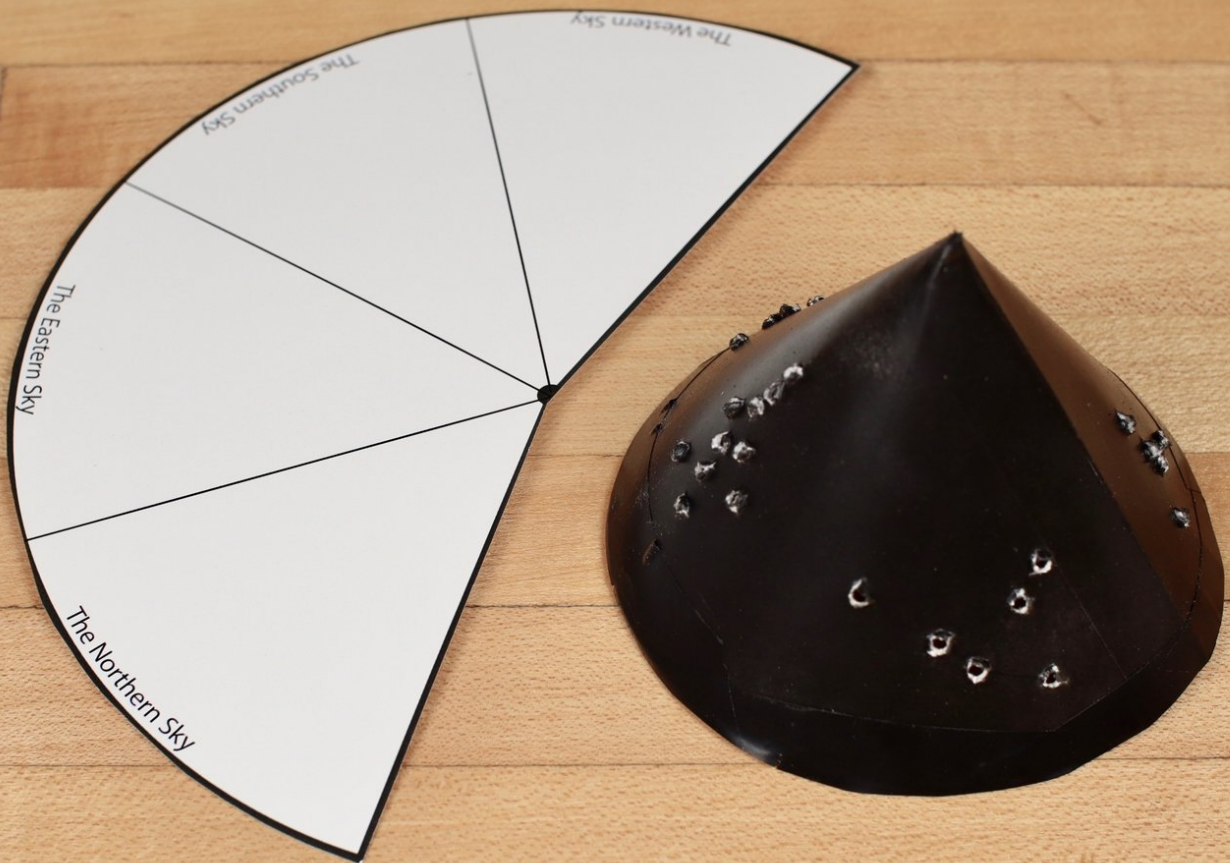




# Sky Cone Transistor

Make a simple dark detecting circuit and constellation cone to make a night sky circuit that turns on when it's dark!

Written By: Andy Wallus





## TOOLS:

- [Scissors](#) (1)



## PARTS:

- [2N3904 NPN Transistor](#) (1)
  - [CR2032 Battery](#) (1)
  - [Light Dependent Resistor](#) (1)
  - [1000 Ohm Resistor](#) (1)
  - [Jumbo 10mm Diffused LED](#) (1)
- White
- [Printable Sky Cone Template](#) (1)
  - [Printable Circuit Template](#) (1)

Add new context to the standard dark detecting transistor circuit with the sky cone. Bring your favorite constellations indoors!