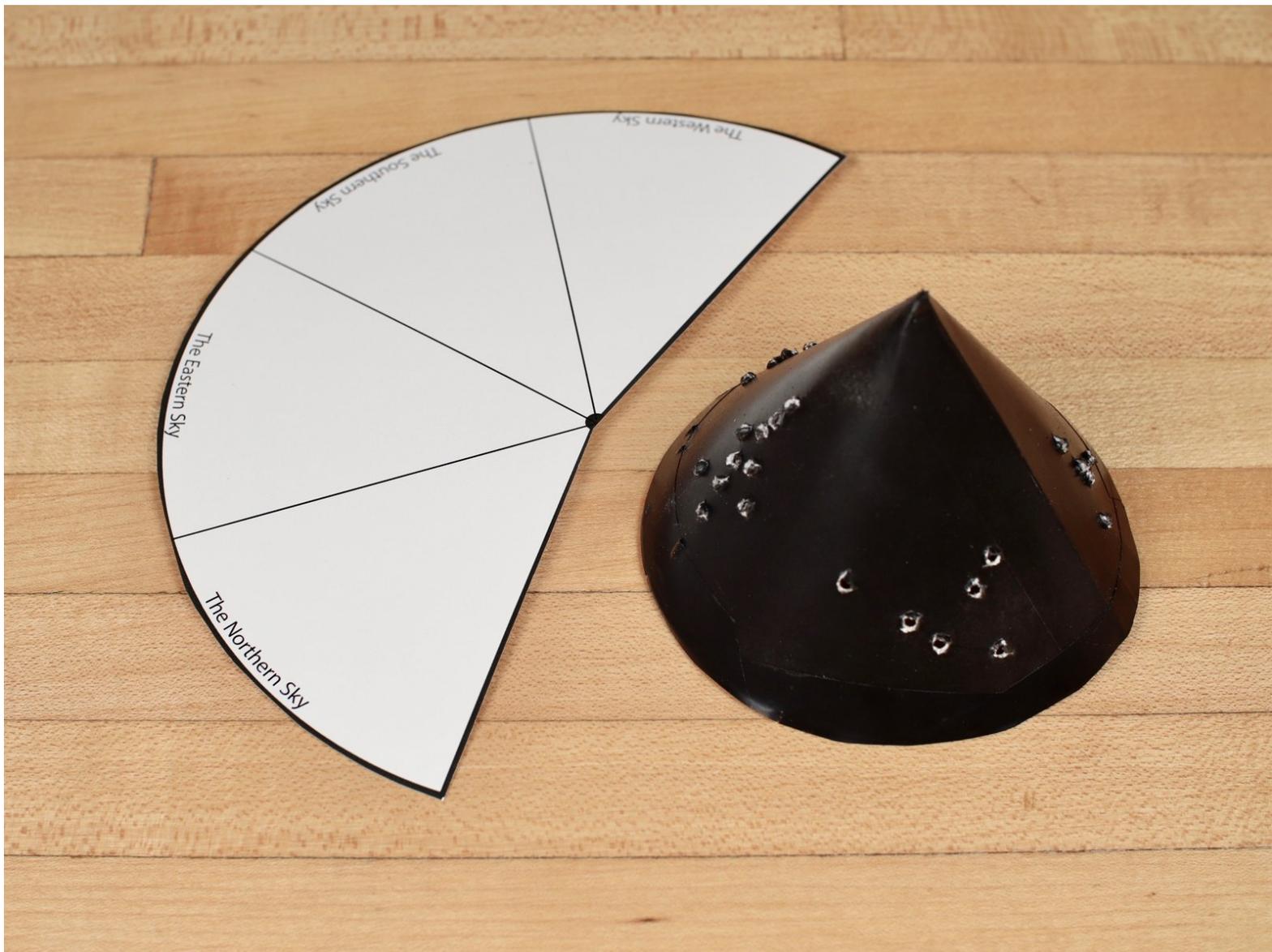




Sky Cone Transistor

Make a simple dark detecting circuit and constellation cone to make a night sky circuit that turns on when it's dark!

Written By: Andy Wallus



INTRODUCTION

Add new context to the standard dark detecting transistor circuit with the sky cone. Bring your favorite constellations indoors!

TOOLS:

- Scissors (1)

PARTS:

- 2N3904 NPN Transistor (1)
- Light Dependent Resistor (1)
- 1000 Ohm Resistor (1)
- Jumbo 10mm Diffused LED (1)
White
- CR2032 Battery (1)
- Printable Template (2)

