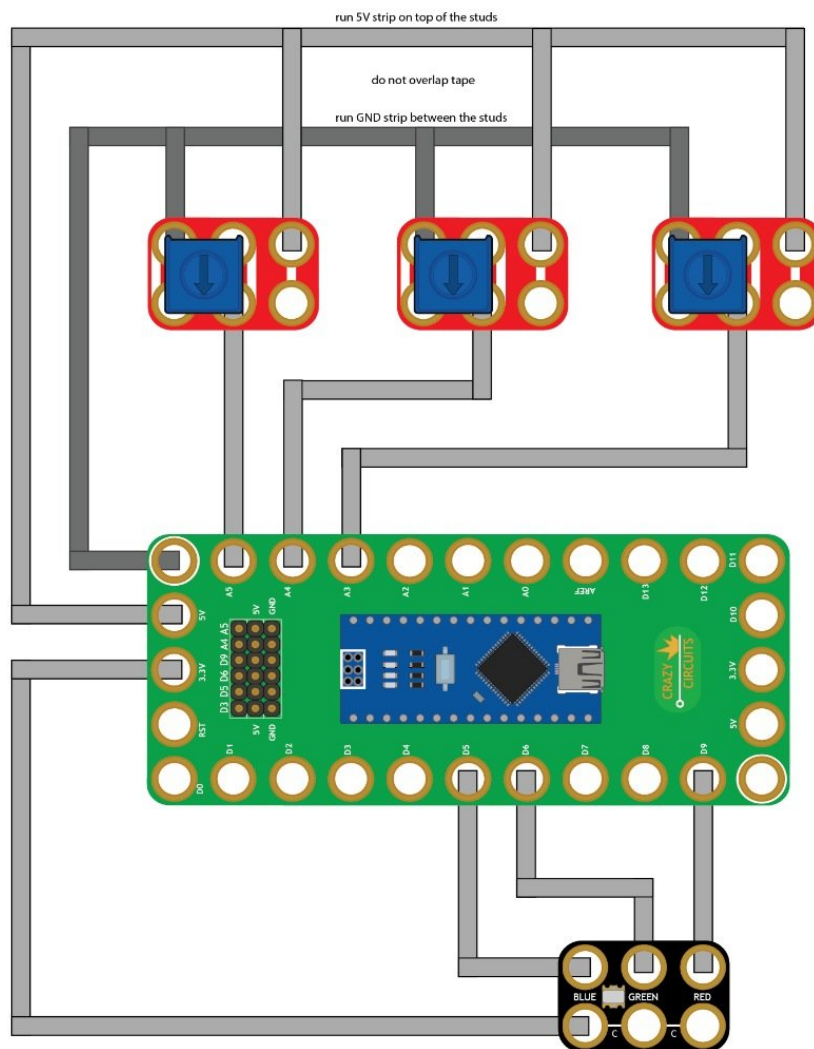




12 - 3 Potentiometers with RGB LED

Use our Programming 101 kit to control and RGB LED with three potentiometers.

Written By: Pete Prodoehl



INTRODUCTION

Use our Robotics Board to control and RGB LED with three potentiometers.



TOOLS:


- [Scissors](#) (1)
- [Computer](#) (1)



PARTS:

- [Crazy Circuits Robotics Board](#) (1)
- [Crazy Circuits Potentiometers](#) (3)
- [Mini RGB LED Chip](#) (1)
- [Maker Tape 1/8th inch](#) (1)

Step 1 — Build the Circuit

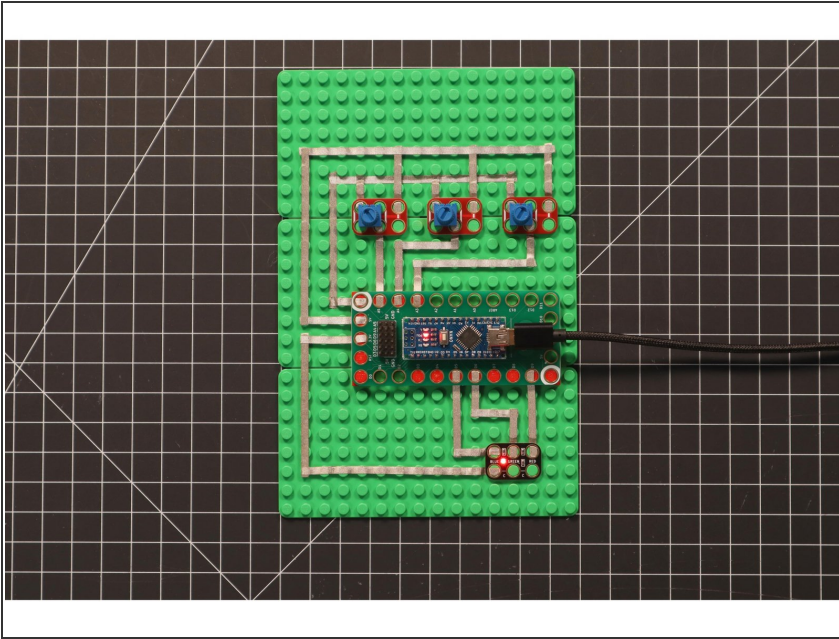

- Build the circuit as shown in the diagram using the components specified.
- ⓘ When connecting the potentiometers, do not cross the tape coming from 5V and GND. (This would create a short circuit.)
- ⓘ You can run the GND tape between the LEGO studs (in the gutter) and the 5V tape on top of the LEGO studs so they do not overlap.

Step 2 — Upload the Code



- Upload the Arduino sketch to the Robotics Board.
- You can find the code here: <https://github.com/BrownDogGadgets/Crazy...>