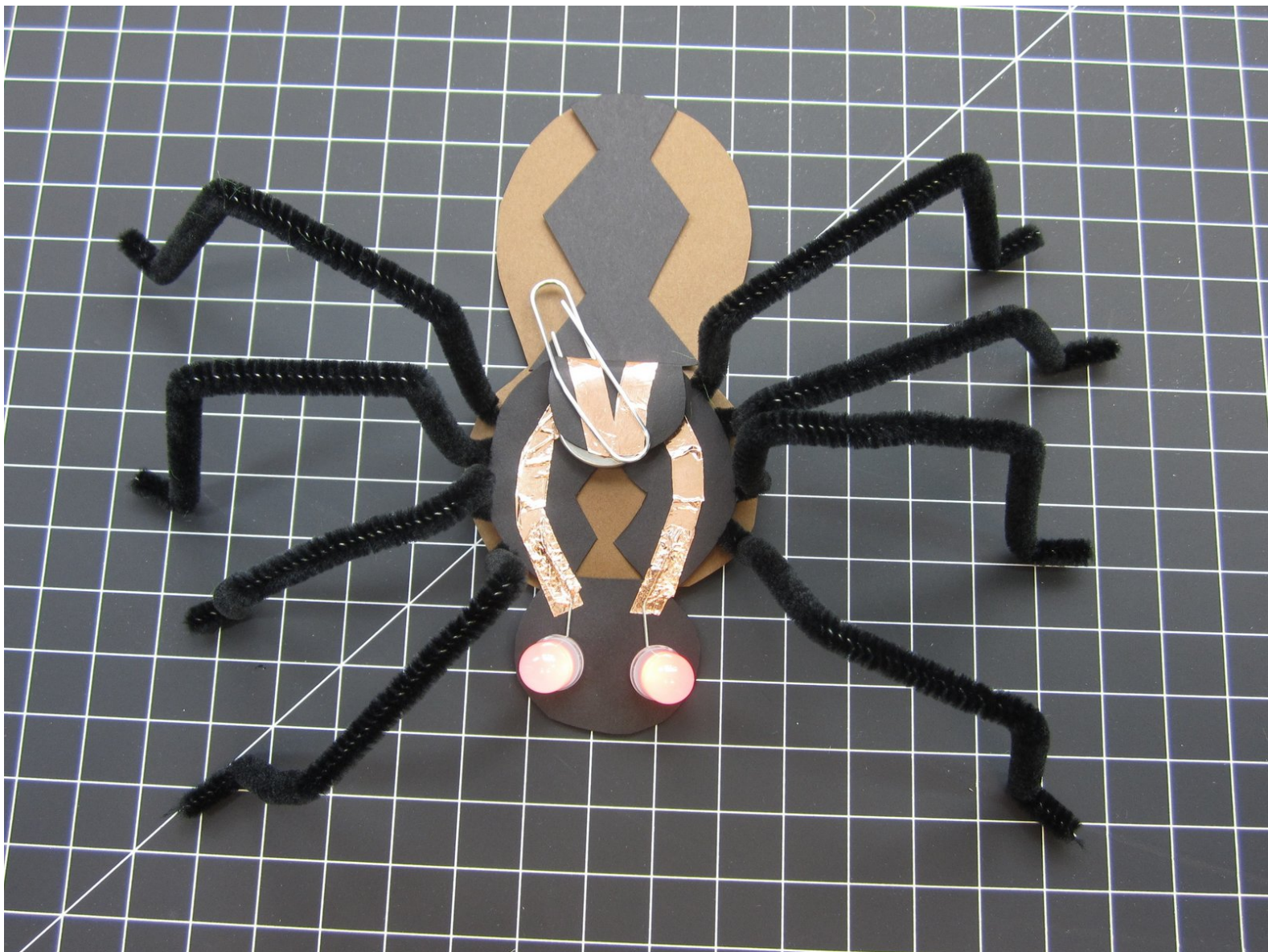




# Spooky Spider 1.0

This spider won't bite you, but it will make Halloween a lot more fun. Create it in minutes using paper and conductive tape.

Written By: Joshua



## INTRODUCTION

This spider won't bite you, but it will make Halloween a lot more fun. Create it in minutes using paper and conductive tape.

Note! This is an older project. Be sure to check out an updated version of this project that uses Maker Tape: [Spooky Spider 2.0](#)



### TOOLS:



- [Scissors](#) (1)
- [Clear Tape](#) (1)
- [Black Pipe Cleaners](#) (1)



### PARTS:

- [Paper Circuits Kit](#) (1)

## Step 1 — Cut Out the Body

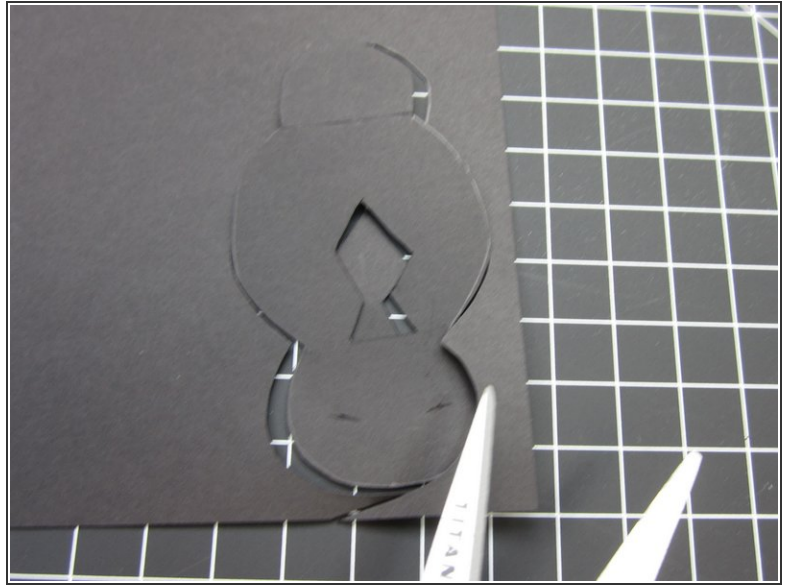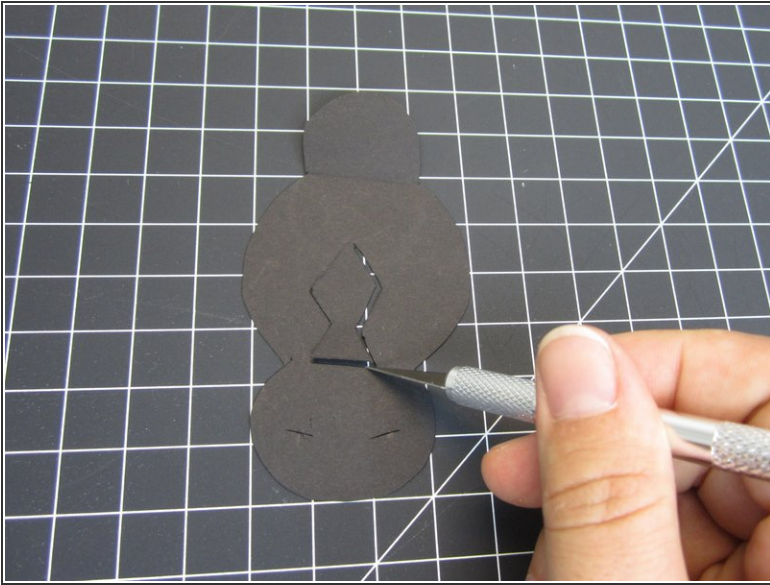


**⚠ Note!** This is an older project. Be sure to check out an updated version of this project that uses Maker Tape: [Spooky Spider 2.0](#)

- Print off the template, trace it, and cut out your spider body parts.
- If you plan on freehand cutting your body, be sure to read all the directions first. Pay special attention to how we create the battery holder.




## Step 2 — Add the LEDs

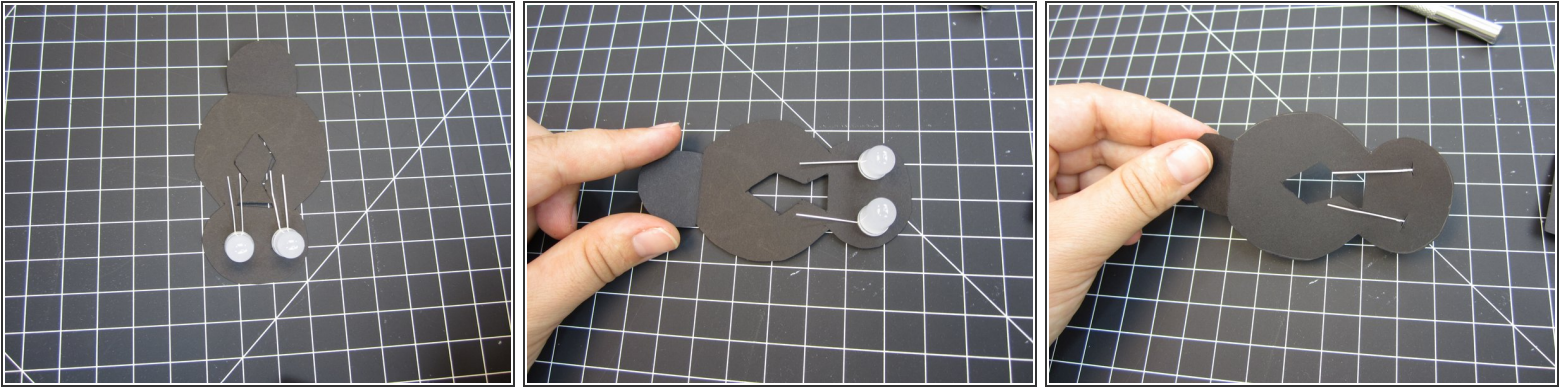

**i** The long leg of an LED is Positive, and the short leg is Negative. For this project the Positive legs go on the bottom, and the Negative legs go on the top.

- Bend both LED legs 90 degrees.
- Stick the long Positive legs through the paper. It may help to cut a small slit in the paper.


## Step 3 — Add the Negative Tape

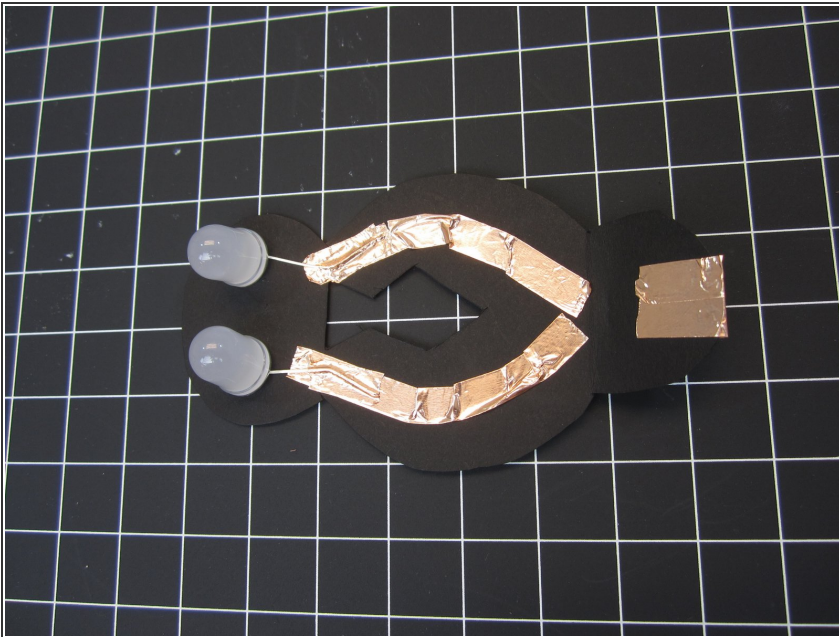

- Run two pieces of tape along the top of your project.
- Stop right next to the ball at the end.


**⚠** The two top pieces can touch, though they should **not** touch the tape from the backside.

## Step 4 — Add the Positive Tape

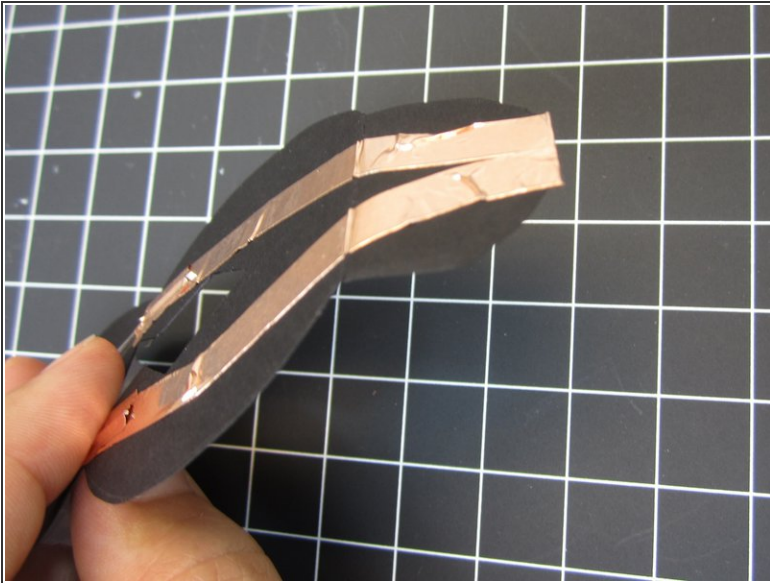

- Run lines of tape from the Positive LED legs back round to the front.
- Do not connect the Positive and Negative tape lines. This will cause a short circuit.



## Step 5 — Tape Down LED Legs

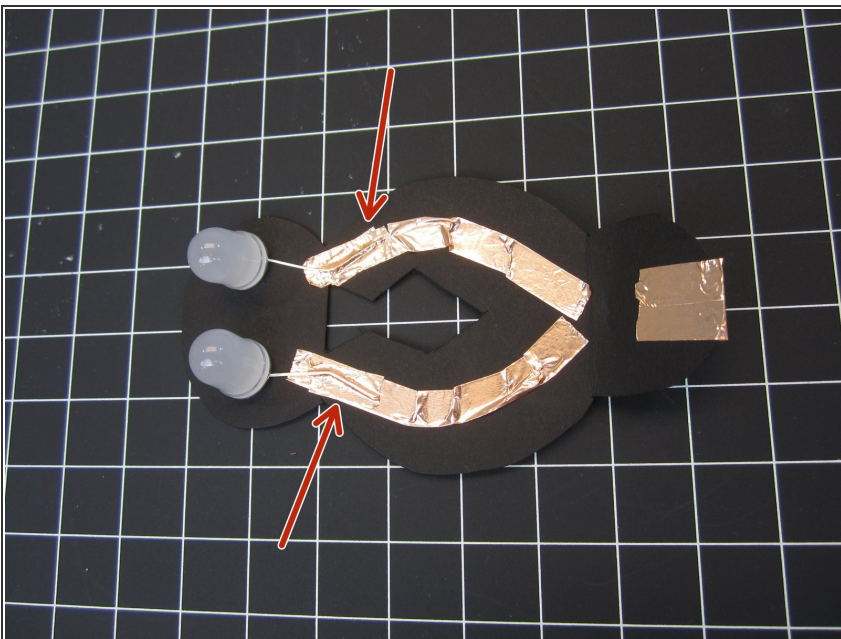

- Position your LED legs over each of the lines of tape.
- Use a small piece of Conductive Tape to tape down each of the legs.
- Do this to all four LED legs.




## Step 6 — Test with a Battery

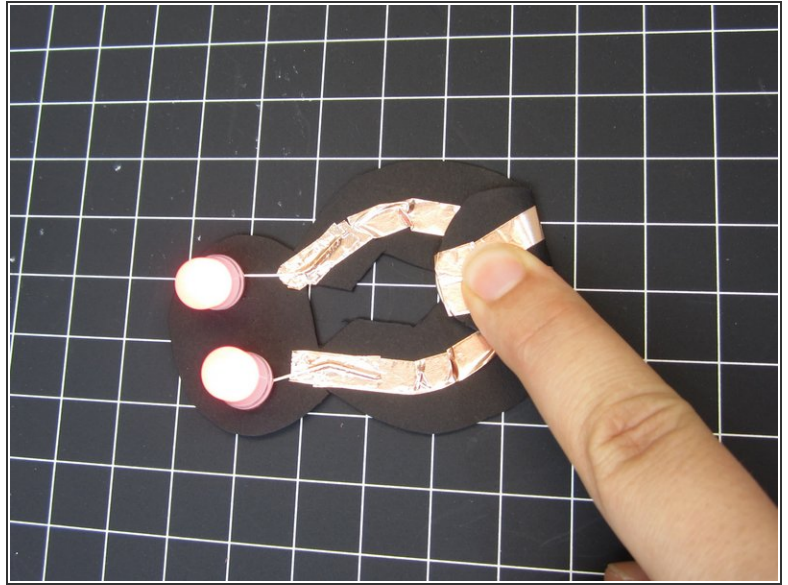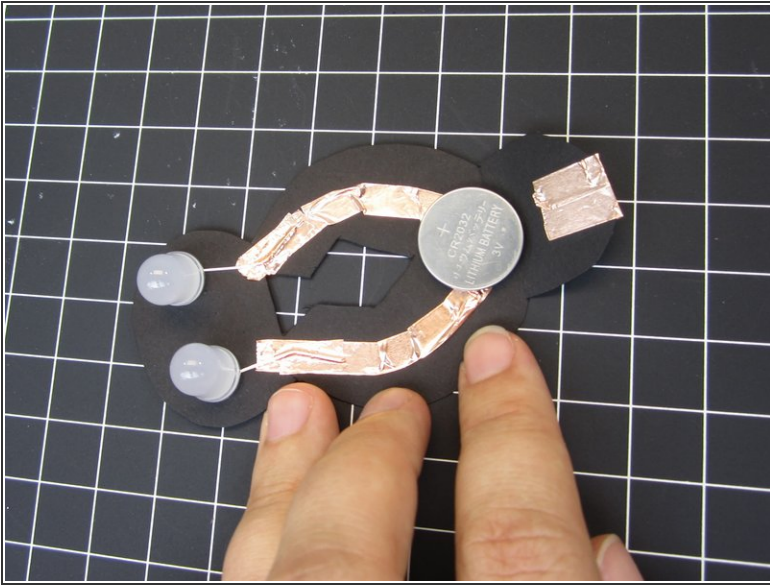


- Place a battery so that bottom (Negative) side is over the two Negative lines of tape. (Top side)
  - Fold down the bulb on the back so that the two Positive lines of tape make contact with the top of the battery.
  - Both LEDs should turn on.
- i** When in doubt, flip the battery over and try again. This solves 90% of all building errors.

## Step 7 — Add Additional Body Parts

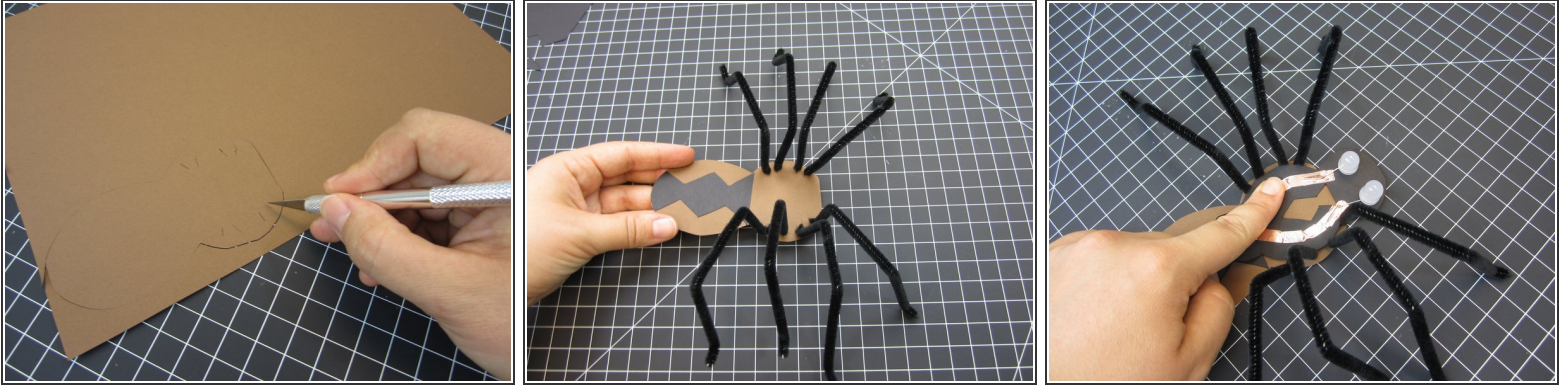

- Cut out the rest of the Spider Body
- Add Legs
- Use tape or glue to connect it to the main body.

## Step 8 — Clip Down The Battery

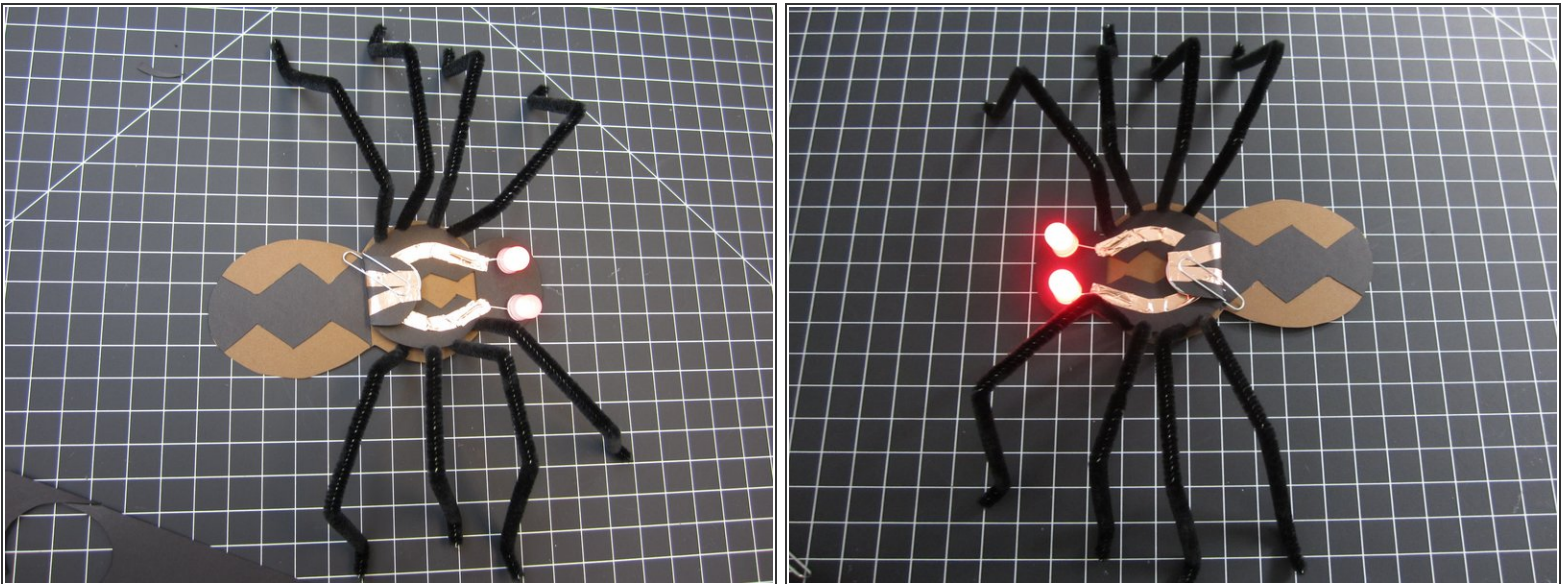

- Use a binder clip or paper clip to hold the battery holder closed.
- Enjoy!