



Headphone Jack

Written By: Pete Prodoehl



INTRODUCTION

Connecting a headphone jack to a Crazy Circuits project allows you to attach computer speakers or headphones for sound output.



TOOLS:


- [Slotted Screwdriver](#) (1)



PARTS:

- [Headphone Jack](#) (1)
- [Crazy Circuits Screw Terminal Chip](#) (1)
- [Maker Tape](#) (1)
1/8" Wide



Step 1 — Hello, Jack!

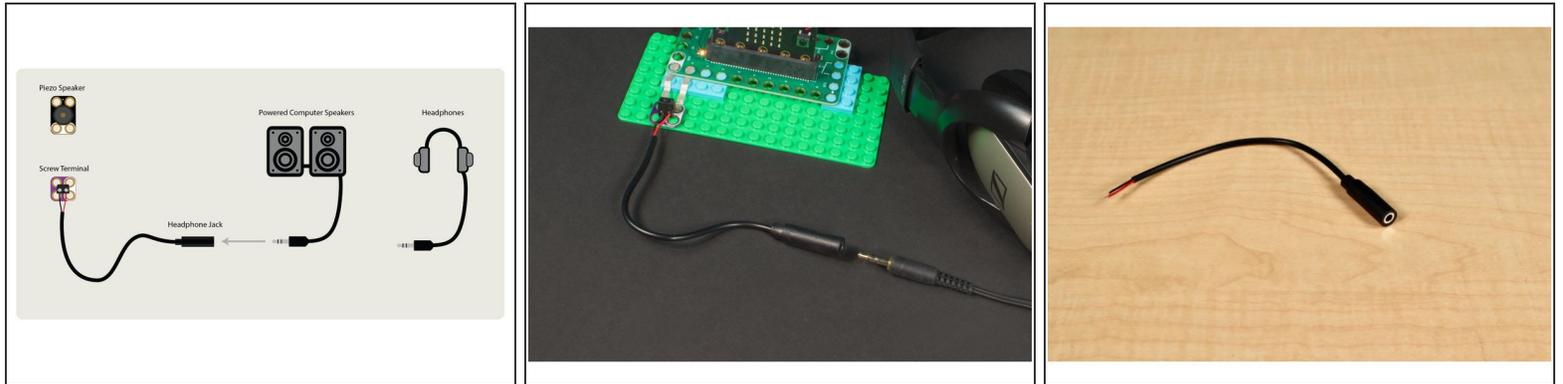

- No matter which Crazy Circuits programming board you use, they can all make sound.
- Using our Piezo Speaker is the simplest way to hear something. Connecting it with a few pieces of Maker Tape is quick and easy.
- If you want to use powered computer speakers, headphones, or anything else with a 1/8" audio connector, the [Headphone Jack](#) is the perfect solution.
- We recommend connecting the Headphone Jack wires to a Crazy Circuits Screw Terminal. All you'll need is a small slotted screwdriver.

⚠ Polarity won't really matter when connecting the wires. It's also worth noting this is a mono (not stereo) audio connector, so you'll only get sound from one side of a headphone or one side from a set of stereo speakers.


Step 2 — Bit Board Connection

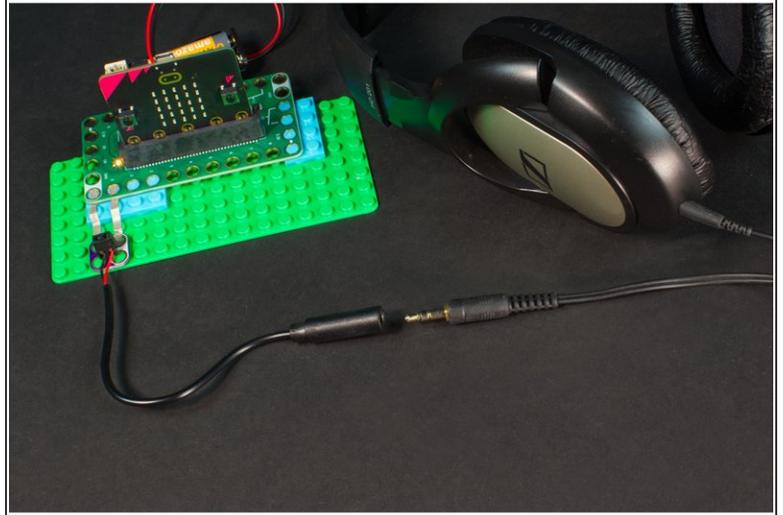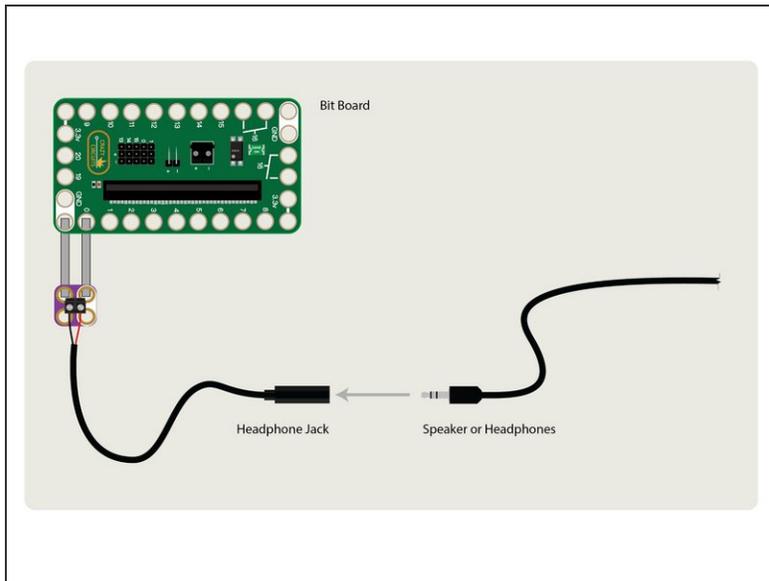

- When connecting to a Bit Board with a micro:bit the default connection will be to **Pin 0** and **GND**.


(i) (Don't worry though, defaults can be changed!)

Step 3 — Bit Board Code

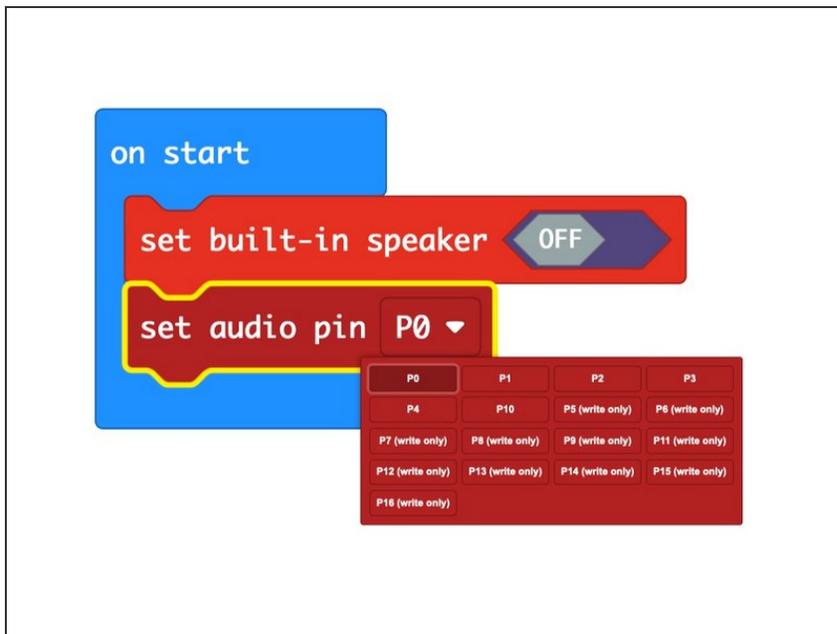


- If you are using a micro:bit V2 it does have an on-board piezo speaker, which you can turn **OFF** in your code.
- You can also specify the pin used for audio output. (If you do not specify one, **Pin 0** will be used.)

Step 4 — Robotics Board Connection

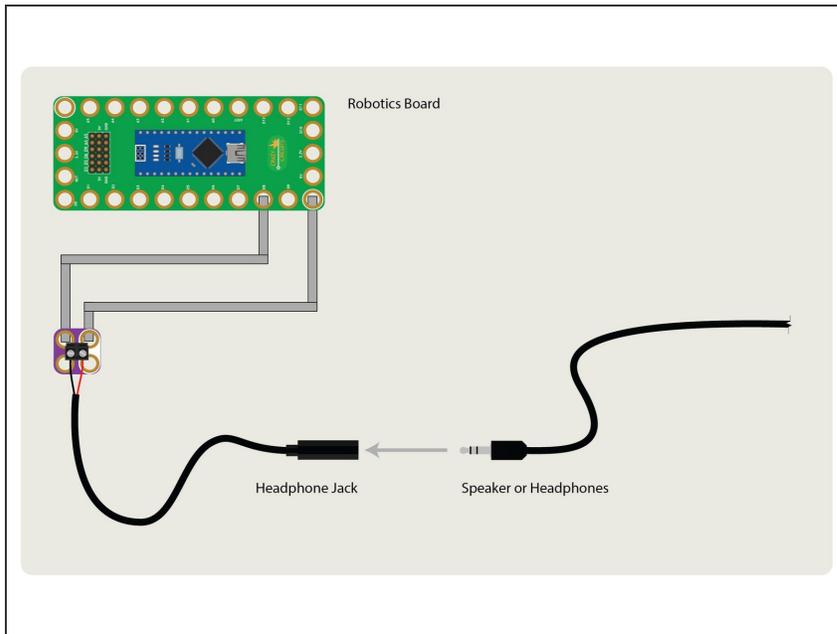

- For the Robotics Board just connect to **GND** and any digital pin.
- Learn more about the [tone\(\) function](#) for Arduino.

Step 5 — Invention Board Connection

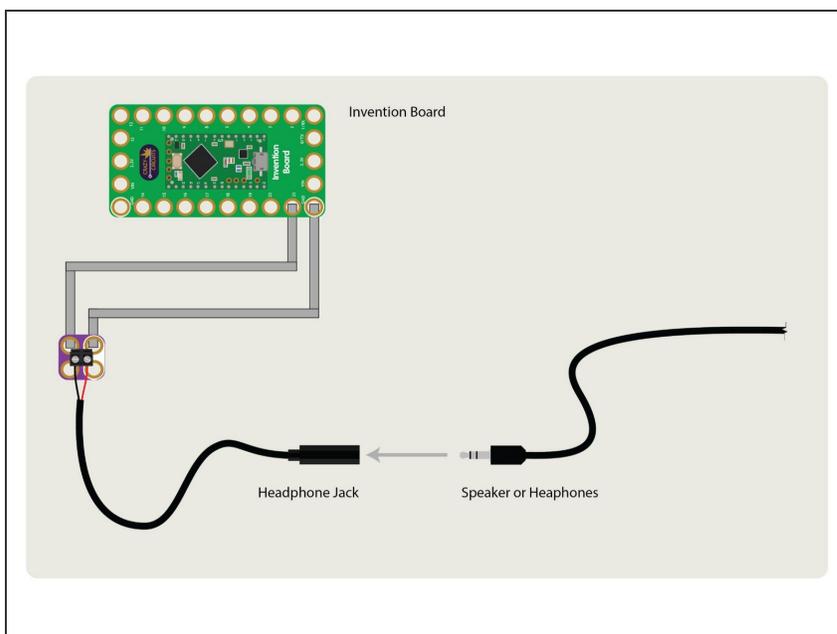

- For the Invention Board just connect to **GND** and any digital pin.
- Learn more about the [tone\(\) function](#) for Arduino.