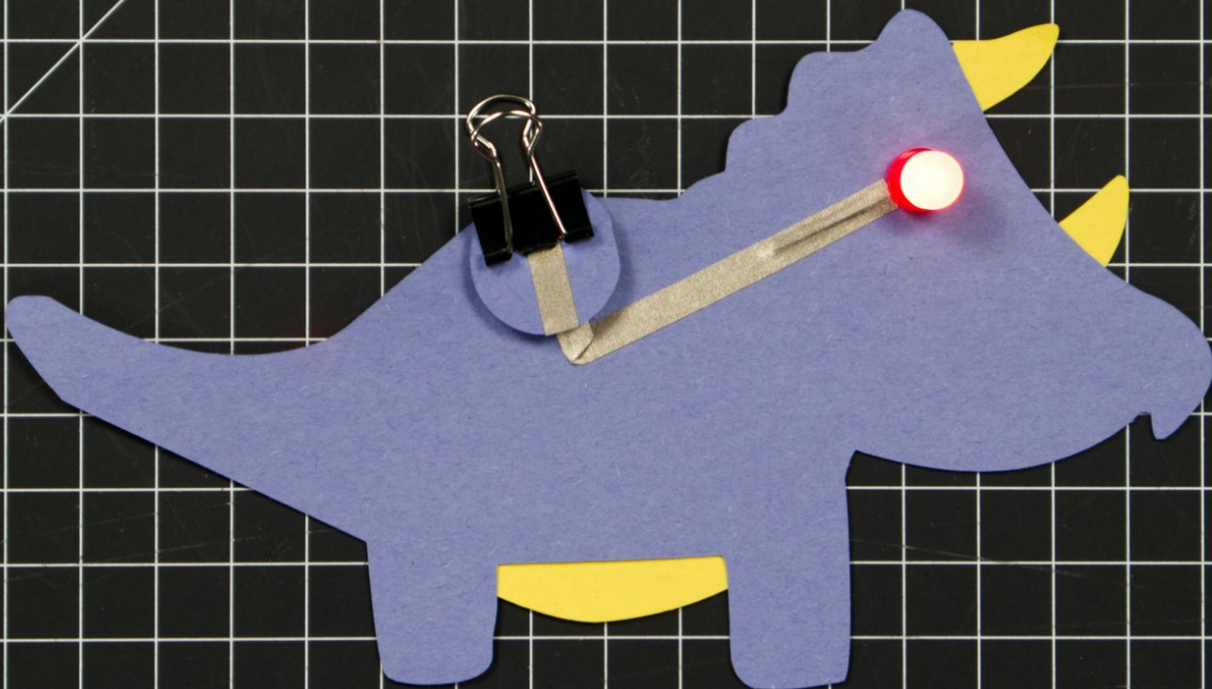




Triceratops

Create your very own paper craft Triceratops Dino Friend using conductive tape and LEDs.

Written By: Joshua



INTRODUCTION

The Triceratops is known for its large head with three horns, but for our paper version we'll add an LED to light things up!



TOOLS:


- [Scissors](#) (1)
- [Tape](#) (1)
- [Glue Stick](#) (1)



PARTS:


- [Paper Circuits Kit](#) (1)

Step 1 — Cut Out the Body

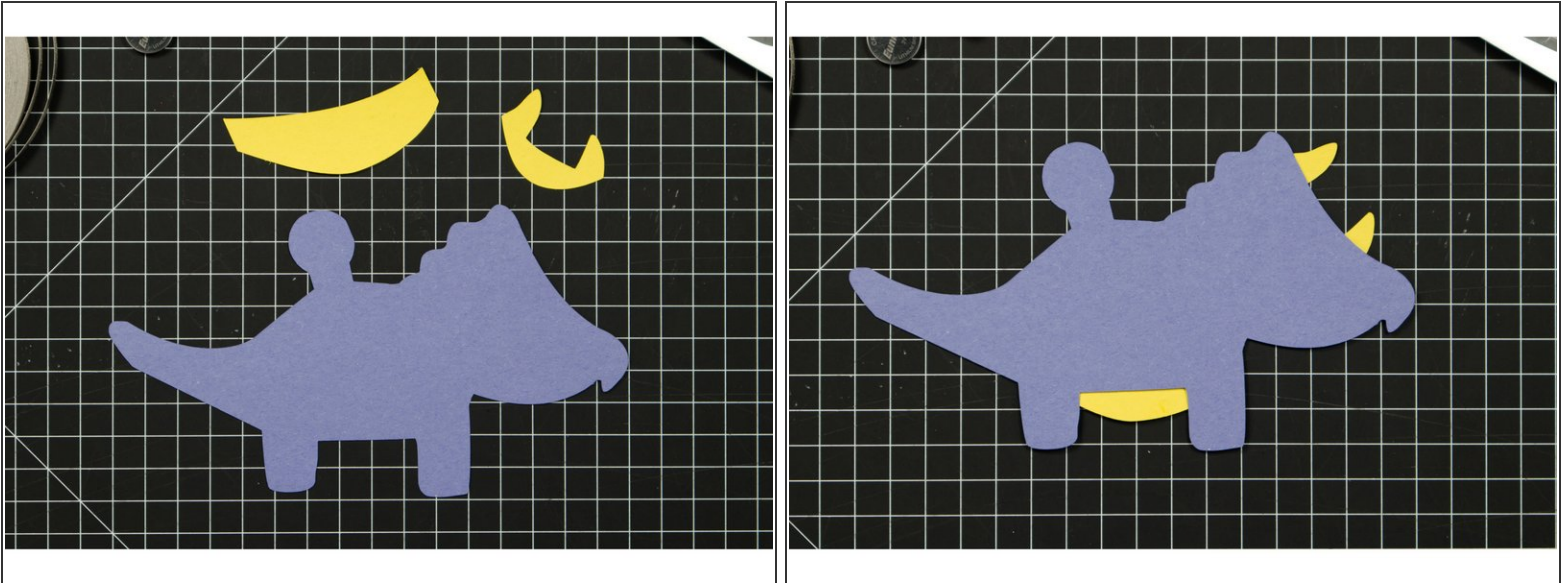


- Print off the template, trace it, and cut out your Triceratops body parts.
- If you plan on freehand cutting your body, be sure to read all the directions first. Pay special attention to how we create the battery holder.

Step 2 — Add the LED

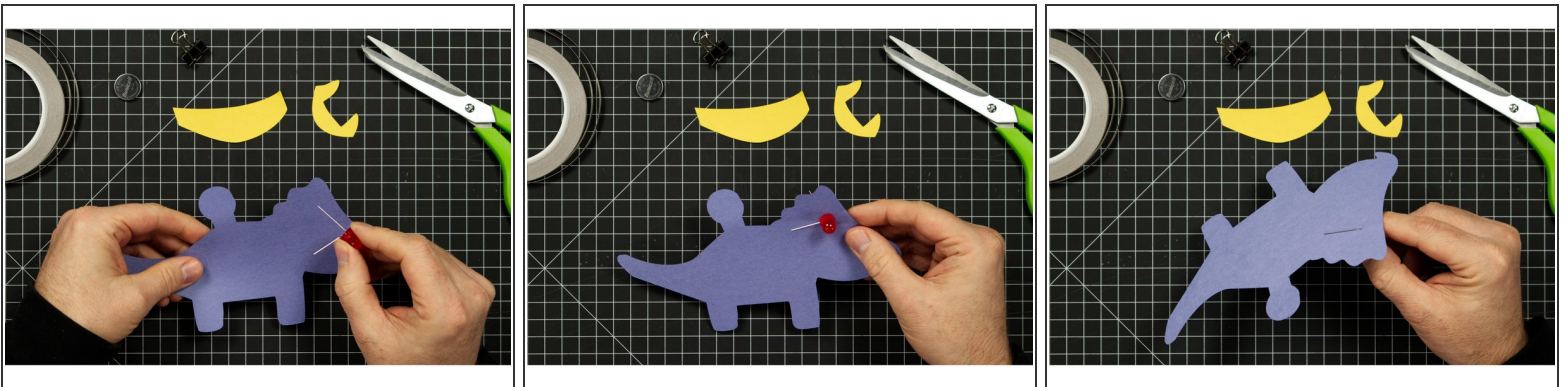


- i** The long leg of an LED is **positive**, and the short leg is **negative**. For this project the **positive** leg goes on the back, and the **negative** leg goes on the front.
- Bend both LED legs 90 degrees.
 - Stick the long **positive** leg through the paper. It may help to cut a small slit in the paper.

Step 3 — Add the Negative Tape

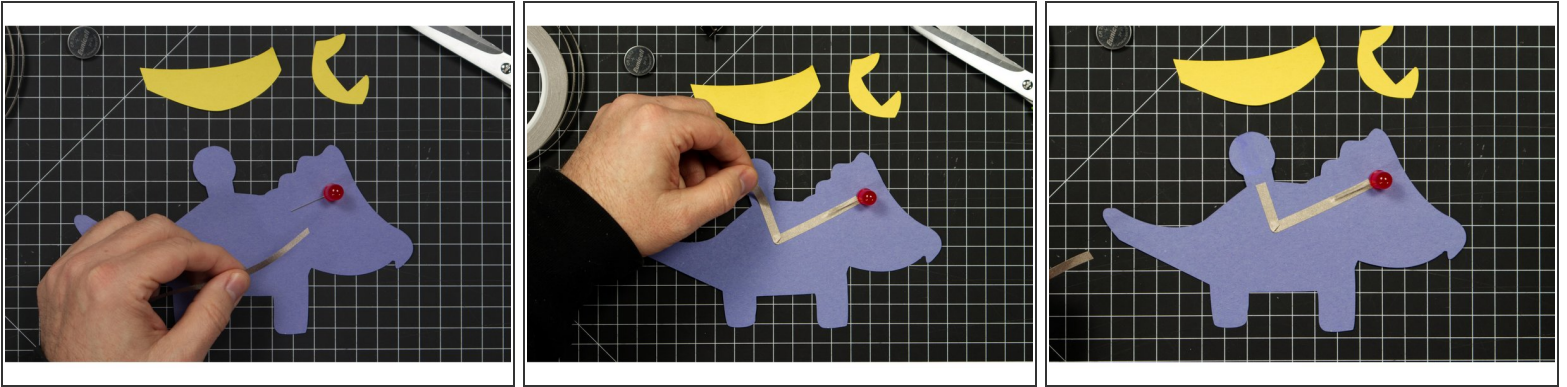

- Run a piece of tape along the front of your Triceratops, covering the negative LED leg.



Step 4 — Add the Positive Tape

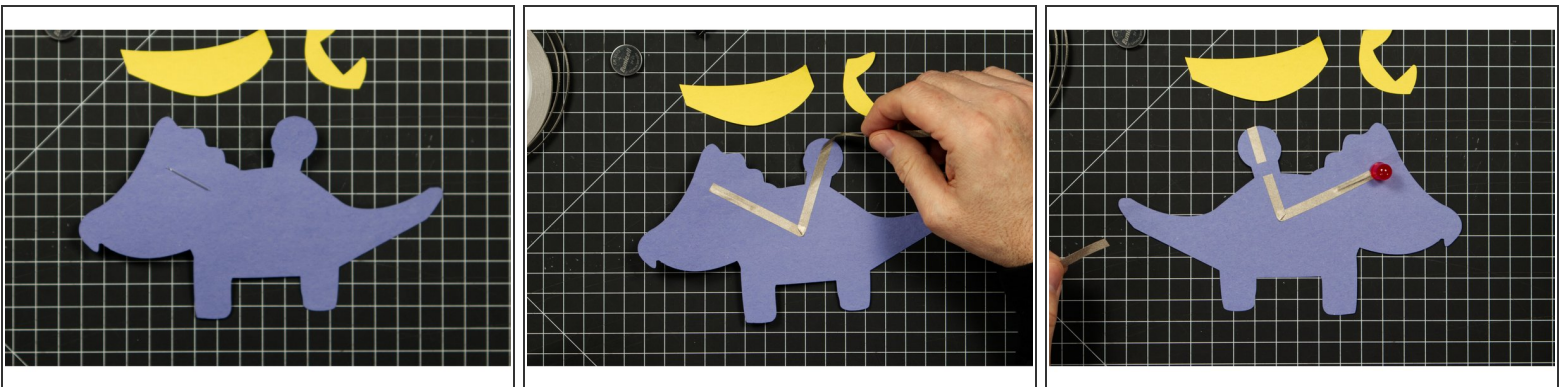

- Run a piece of tape covering the **positive** LED leg, down and then over to the round battery holder piece.
- The tape should wrap around the round part to the front side of the Triceratops.
- You can choose to make a right angle turn or overlap multiple pieces of tape. Either method will work with Make Tape because it's conductive on all sides.


⚠ Do not connect the positive and negative tape lines. Doing so would cause a *short circuit*.

Step 5 — Test with a Battery

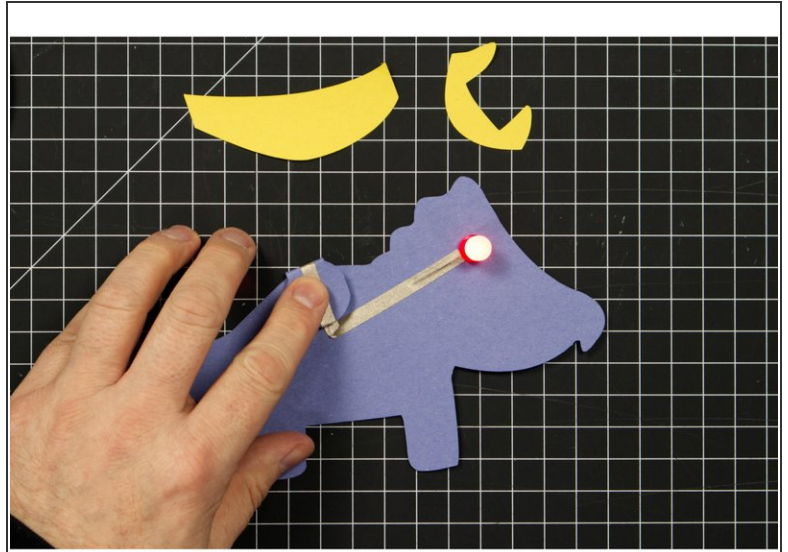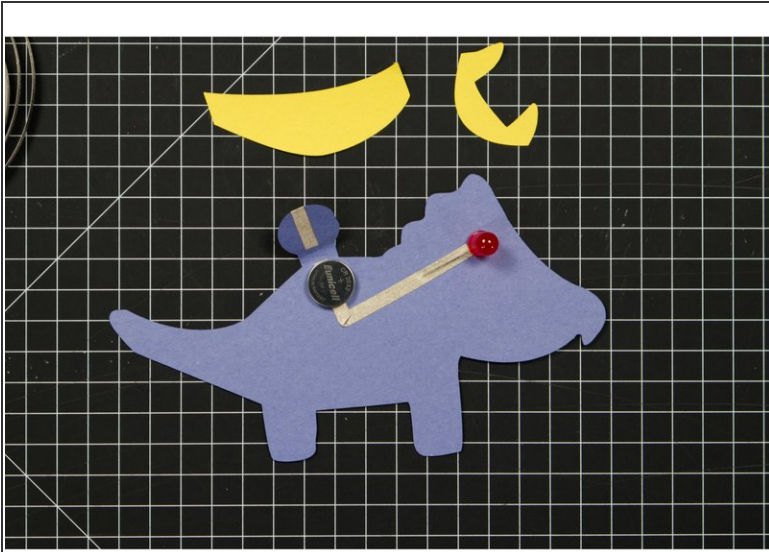




- Place the battery so that bottom (negative) side is over the negative line of tape.
 - Fold down the round battery holder section on the back so that the positive line of tape make contact with the top of the battery.
 - The LED should turn on!
- i** If your LED does not light up, try flipping the battery over. If it still does not light up, make sure your tape is pressed down securely against the LED legs.

Step 6 — Add a Binder Clip

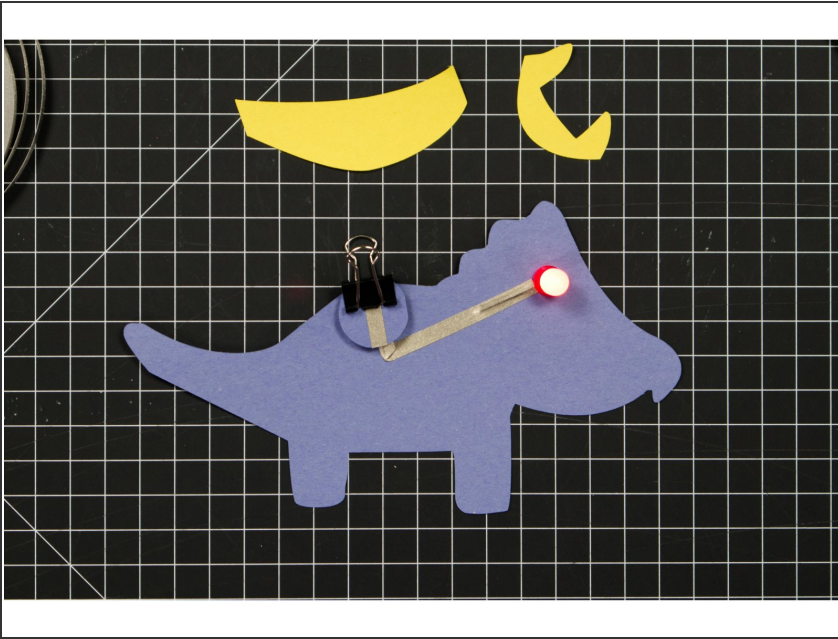


- Use a binder clip to hold the battery in place.
- To "Turn Off" the project, just remove the binder clip.

Step 7 — Decorate

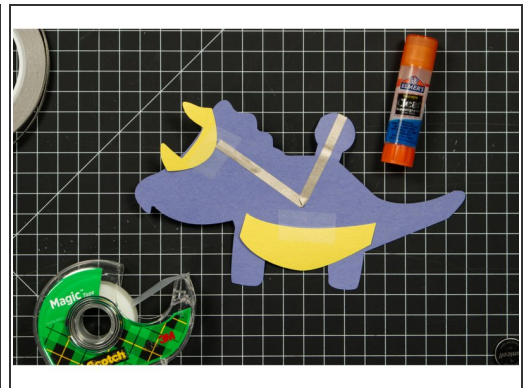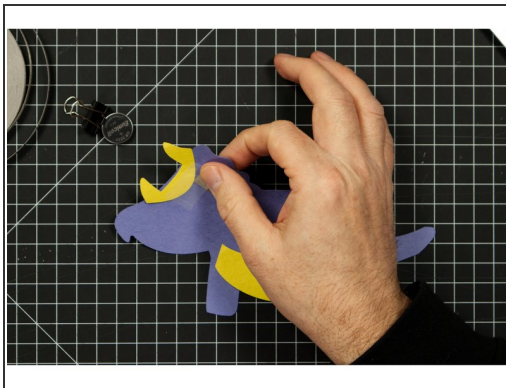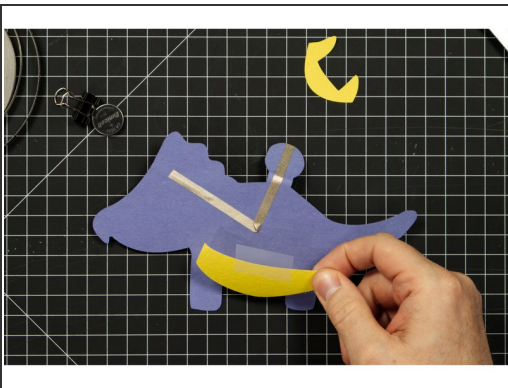


- Add on the rest of the body parts using glue or tape.
- Your Dino Friend is now complete... Enjoy!

Step 8 — Tip - Use a Tape Loop

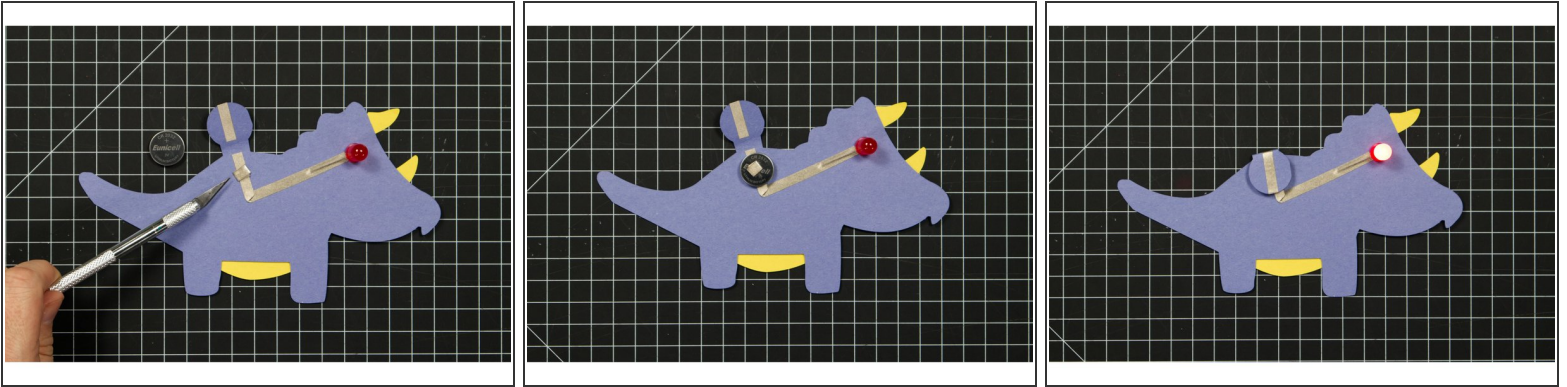

- Since Maker Tape is conductive on both sides you can use it to make a tape loop that helps hold your battery in place.
- If you wanted to, you could use two tape loops (one for each side of the battery) and turn on and off your circuit without the need of a binder clip.

Step 9 — Make More Friends!

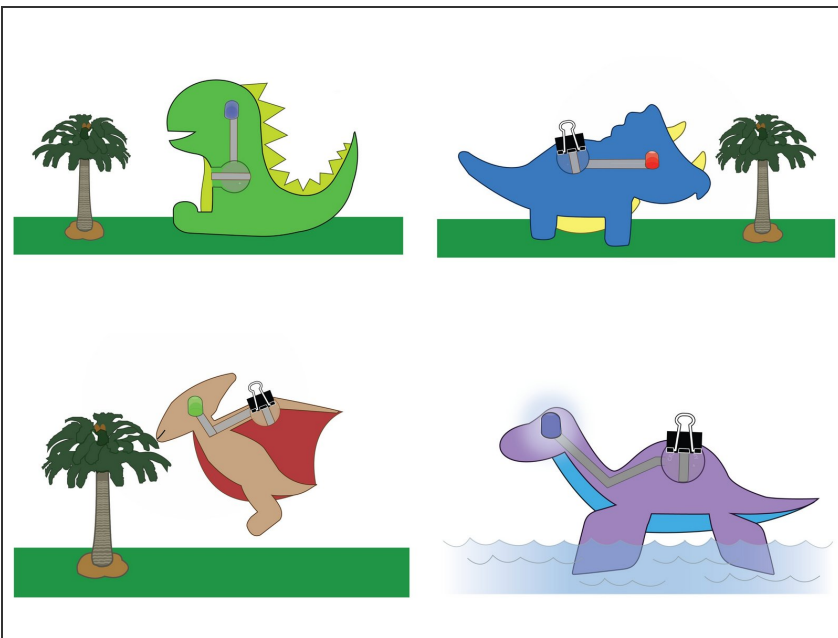

- Check out our other Dino Friends; [T-Rex](#), [Pterodactyl](#), and [Plesiosaurus](#).