



# Thanksgiving Awards

Complete this set of light-up awards and hand them out to the champions of your Thanksgiving Feast this year!

Written By: Andy Wallus



## INTRODUCTION

Complete this set of light-up awards and hand them out to the champions of your Thanksgiving Feast this year!

There are full-color versions as well as a black & white versions that makes a great coloring activity.

You can make this project (and many more!) with our **Paper Circuits Kit**.


### TOOLS:

- [Scissors](#) (1)
- [Markers, Crayons, or Colored Pencils](#) (1)
- [Push Pin](#) (1)

### PARTS:

- [Paper Circuits Kit](#) (1)
- [Printable Template](#) (1)



## Step 1 — Gather Materials

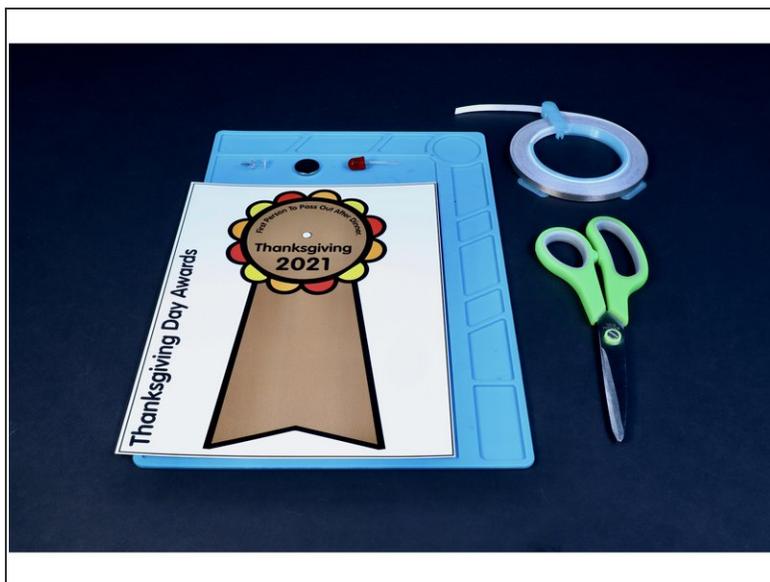

**⚠ Note:** We originally made these for Thanksgiving 2021 but they were so popular we updated them (by removing 2021) to be for **every year!**



- **Gather the materials** listed in this guide and **print out whichever templates you wish to complete.** Note: There are colored and blank versions of each award.
- If you chose to complete blank projects, **color them as you wish** with crayons, markers or colored pencils. Once this is done **OR** if you chose the already colored versions, **cut out your project(s).**

## Step 2 — Poke Holes

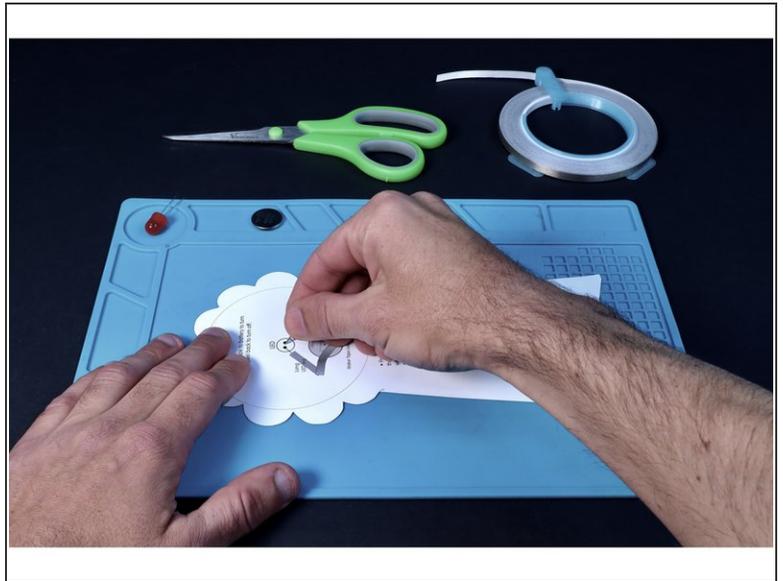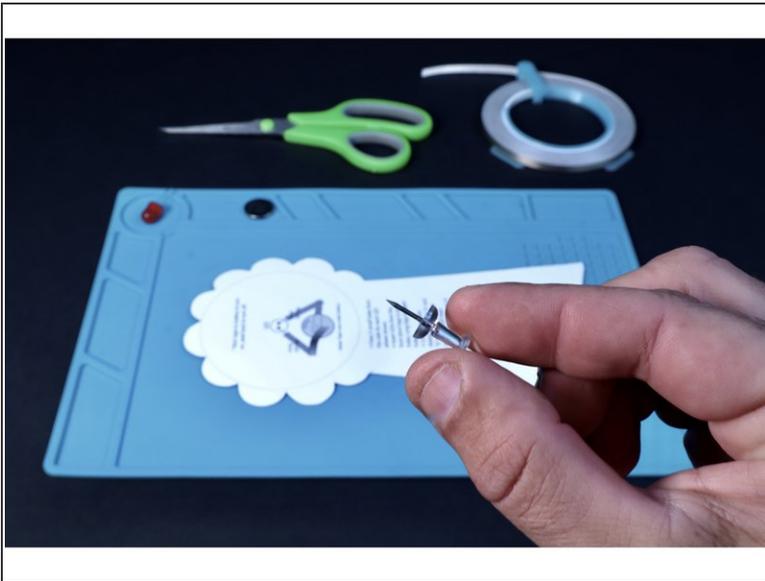




- **Flip your project to the circuit diagram side.** Use a thumbtack or pushpin to **poke two holes for the LED legs** where shown on the diagram with small black dots.

### Step 3 — Add LEDs

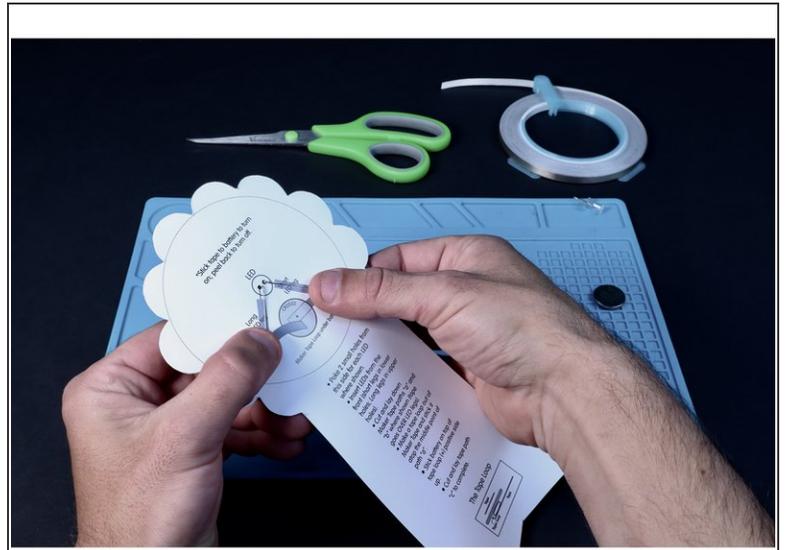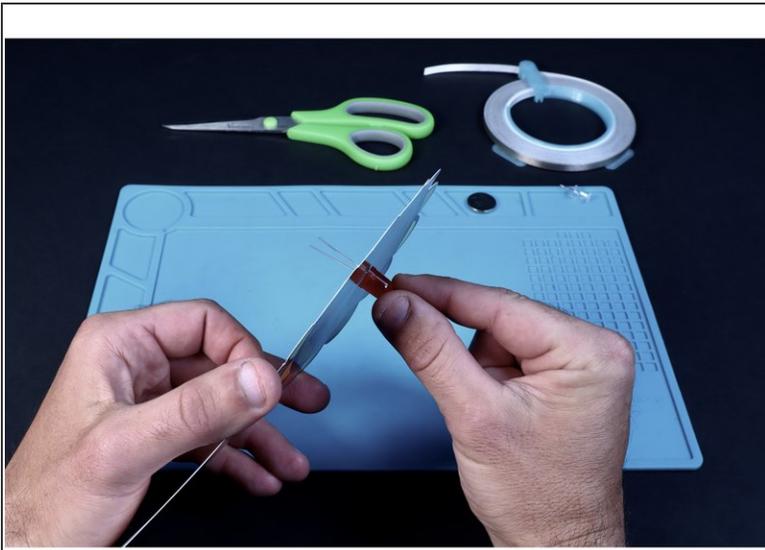


- **Thread the LED legs** through those two holes from the front as shown. **Take care** to insert the long LED leg into the right hole (when viewed from the front) and the shorter LED leg into the left hole.
- Flip the project around and **bend the LED legs** as indicated on the diagram.

## Step 4 — Add Maker Tape

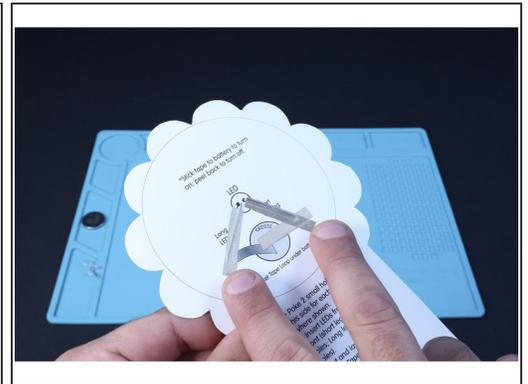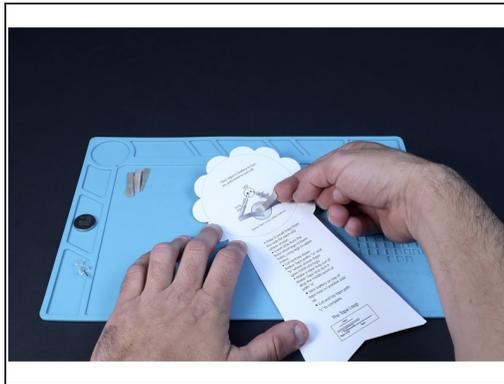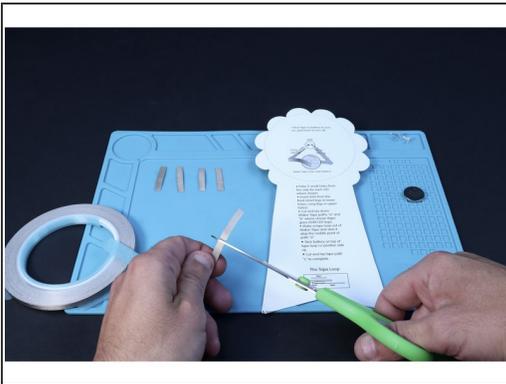

- Use the circuit diagram and a scissors to help you measure and **cut four small pieces of Maker Tape**.
- **Peel and stick a Maker Tape path** from atop the battery graphic right, toward the short leg path.
- **Peel and stick a Maker Tape path atop each of the LED legs** where shown on the diagram. The short leg path should connect to the first path you placed.

## Step 5 — Add Tape Loop and Battery

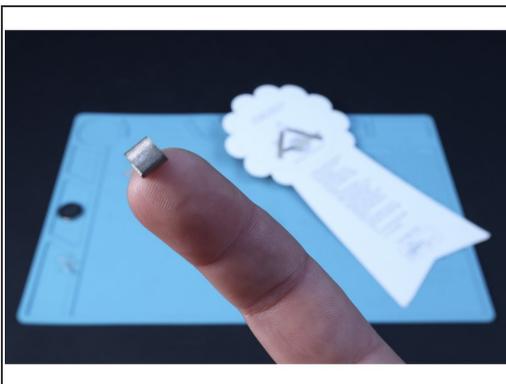

- Use of the remaining Maker Tape segment to **make a tape loop**.
- **Stick the tape loop to the end of the tape path atop the battery graphic** as shown in the second photo.
- **Stick the battery atop the tape loop** with the positive (+) side facing UP.

## Step 6 — Add Last Piece of Maker Tape



- **Peel and stick the final Maker Tape path** that leads from the long leg path to the top of the the battery as shown.
- **NOTE:** Connecting this final tape path will compete your circuit and turn the LED on the opposite side ON, while peeling it back will turn the LED OFF.
- **Complete them all** while you're waiting for dinner to be served and **hand them out afterward** to whoever deserves them!

Complete them all while you're waiting for dinner to be served and hand them out afterward to whoever deserves them!