



# Stella Star

Make your own "Stella Star" a light-up paper circuit project using two LEDs, a CR2032 battery, and some Maker Tape.

Written By: Pete Prodoehl



---

## INTRODUCTION

Make your own "Stella Star" a light-up paper circuit project using two LEDs, a CR2032 battery, and some Maker Tape.

There's a full-color version as well as a black & white version that makes a great coloring activity.

You can make this project (and many more!) with our **Paper Circuits Kit**.



### TOOLS:

- [Scissors](#) (1)
- [Safety Pin](#) (1)



### PARTS:


- [Paper Circuits Kit](#) (1)
-

## Step 1 — Print and Cut



- Print out the template.
- You can choose to cut out the star for a cleaner look, or just leave it as-is with the instructions on the page.
- ① If you use the black & white version it's best to color it before you cut it out.
- ① We recommend printing the file on a heavier paper like cardstock.
- ① For best results cut from the front side in case your print doesn't line up properly with the back.
- ① It makes things easier if you can print double sided, but you can just print the front and use the back side as a guide to build your circuit.

## Step 2 — Add LEDs

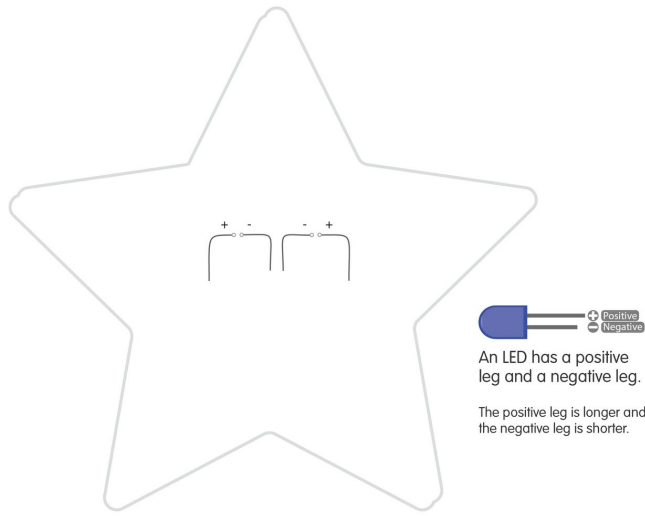



- Poke holes through the front for the LED legs. (We recommend using a safety pin, paper clip, or thumbtack.)
- Insert the LED legs through the front, making sure the negative legs are towards the center. (The shorter LED leg is the negative one.)
- Bend the LED legs flat against the back side.

## Step 3 — Add Negative Side Maker Tape






- Add the center piece of Maker Tape to the LED legs. (This will connect the negative legs to the negative side of the battery.)
- ❗ If you need to use more than one piece of Maker Tape to connect them that's fine. You can overlap Maker Tape and it will still work because it's conductive on both sides and all the way through.
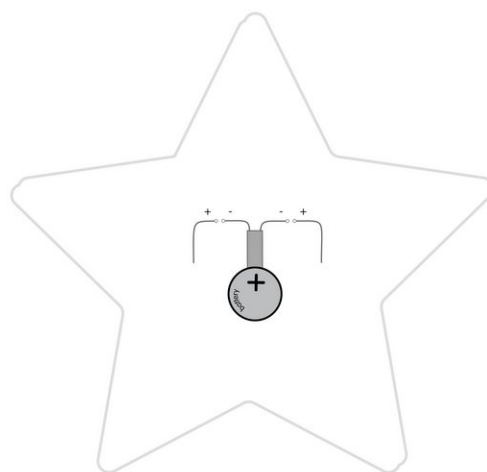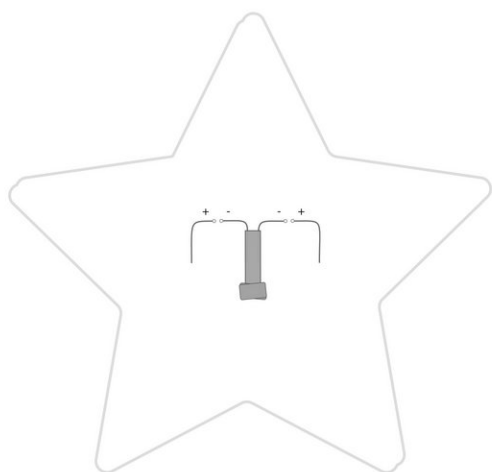
## Step 4 — Add the Tape Loop and Battery



- Add a tape loop to the center piece of tape, then stick the battery down to it. (Make sure you stick the negative side of the battery down.)

## Step 5 — Add Positive Side Maker Tape

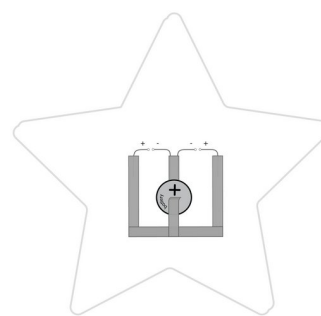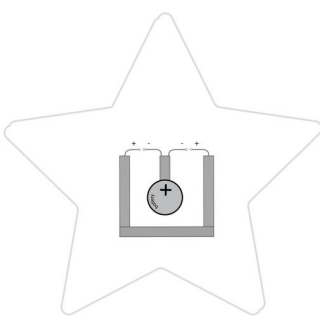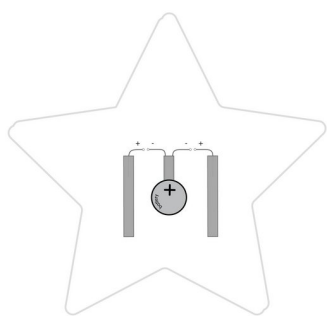

- Add additional pieces of Maker Tape to connect the positive LED legs to the top of the battery.
- Your LEDs should light up as soon as you connect the tape.)
- The final piece of Maker Tape connects to the to top of the battery. This makes it easy to turn off your circuit by just peeling back the tape.

## Step 6 — Enjoy!



- Enjoy your paper circuit!