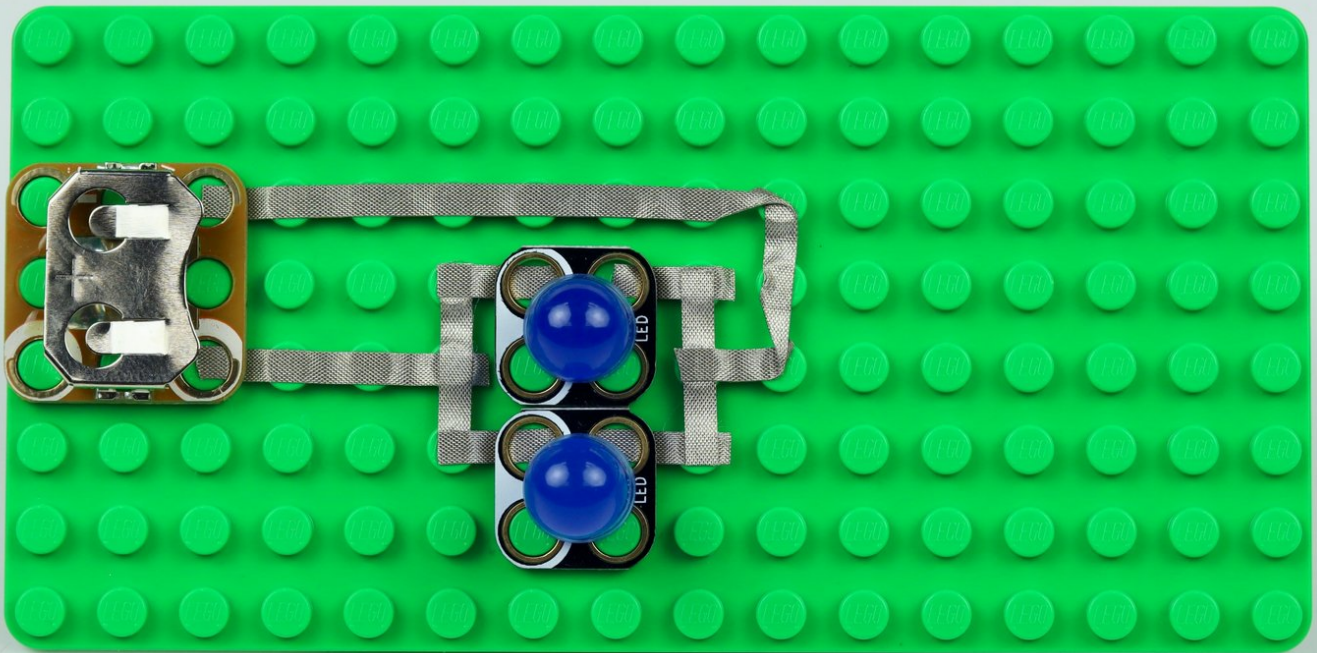




Day 3: Series and Parallel

Explore circuits that allow more than one component to work at the same time. Physically assemble and observe both series and parallel circuits from kit.

Written By: Andy Wallus





TOOLS:

- [Crazy Circuits Classrooms: Circuits 101](#) (1)
- [Scissors](#) (1)
- [Week 2 Day 3 student WS](#) (1)

Students will have assembled a circuit that requires two simultaneous outcomes in two basic forms; series and parallel. Through observation, they will also have begun to understand their characteristics, benefits and limitations.