

Reindeer Card

Create a light-up Holiday card featuring a Reindeer! Just add an LED, a CR2032 battery, and some Maker Tape.

Written By: Pete Prodoehl



INTRODUCTION

Create a light-up Holiday card featuring a Reindeer! Just add an LED, a CR2032 battery, and some Maker Tape.

There's a full-color version as well as a black & white version that makes a great coloring activity.

You can make this project (and many more!) with our Paper Circuits Kit.



TOOLS:

- Scissors (1)
- Safety Pin (1)

Optional

• Push Pin (1)

Optional





PARTS:

Paper Circuits Kit (1)

Step 1 — Make Your Card



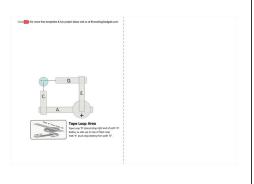

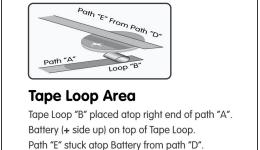

- This paper circuits card is a great beginner project. Just follow the steps below to make your card.
 - Print out the full-color card, or print out the black and white card and color/decorate as desired.
 - Poke holes through the front of the card for the LED legs, then push the legs through the front.
 - Make note of where the Positive and Negative legs go. Polarity matters!
 - On the inside of the card, bend the LED legs down flat against the paper.
 - Add Maker Tape and a Battery to complete your circuit.
- ① Note: If you are using thicker paper (such as cardstock) we recommend using a large safety pin to poke the holes in the paper to put the LED legs through.