

Light-Up Skull Eyes T-Shirt

Make your Halloween skull shirt scarier than ever by adding glowing eyes!

Written By: Natasha Dzurny



INTRODUCTION

Make your Halloween skull shirt scarier than ever by adding glowing eyes! This sewing project uses two LEDs and a Blink/Fade Board to give a shirt glowing eyes. You'll only need simple sewing skills and a little bit of time to create this fun wearable.


TOOLS:	DARTS:
 Scissors (1) 	Crazy Circuits LED Chip (2)
Needle (1)	 Crazy Circuits Blink/Fade Board (1)
 Clear Nail Polish (1) An Aweseomly Scary T-Shirt (1) Sewing Thread (1) 	 Crazy Circuits Coin Cell Battery Holder (1) Conductive Thread (1) crazy circuits switch (1)

Step 1 — Light-Up Skull Eyes T-Shirt




- Gather your materials
- Choose a shirt! We found ours at Target.

Step 2

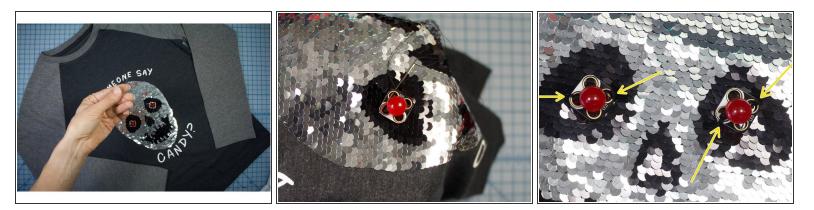

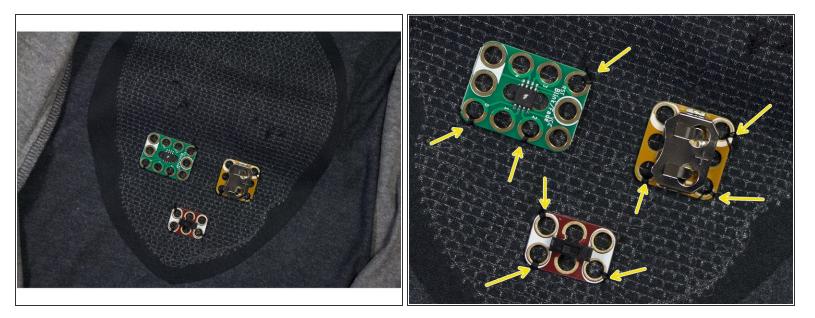- Thread a needle with black thread.
- Place the Red LEDs over the eyes.
- Stitch the LEDs onto the shirt where shown.
 - (i) Tip: It can be a bit tricky to hold the LED, the shirt, and the needle while sewing. Use a tiny piece of double sided tape to tack the LED in place while you are stitching.



- Turn the shirt inside out.
- Tack the other components to the shirt where shown, through at least three of the holes.
- (i) It is important that you place the components exactly as the picture shows. Be sure that the negative side of the battery component and holes 4 & 3 on the blink/fade board are facing up, or toward the collar of the shirt.



- Turn the shirt right side out.
- Thread your needle with conductive thread.
- Sew a few finishing knots to the negative hole of the first red LED to make a good connection. End with the thread on the inside of the shirt. DO NOT cut the thread.

Step 5



- Turn the shirt inside out. Sew a running stitch to the location of the negative hole on the second led.
- End with the thread on the outside of the shirt. DO NOT cut the thread.




- Turn the shirt right side out. Sew a few finishing stitches to the negative hole of the second LED.
- End with the thread on the inside of the shirt. DO NOT cut the thread.

Step 7




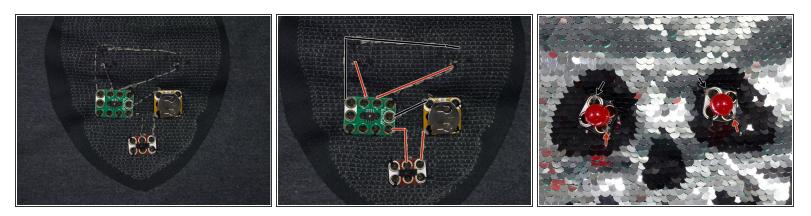• Turn the shirt inside out. Stitch the thread back along the path. Tie a knot and trim the thread as shown.




• Continue to make the rest of the connections as shown.

Step 9

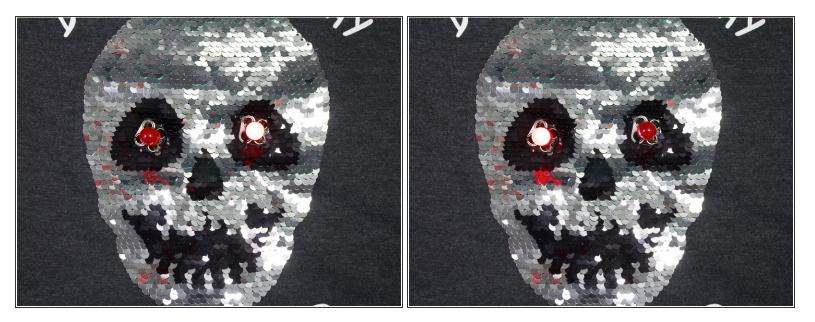

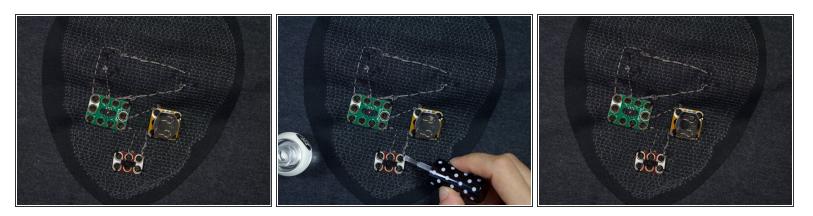- Turn the shirt right side out.
- Turn on the switch you should have a blinking skull!



- Once you have a working circuit, turn the shirt inside out one more time.
- Apply clear nail polish or crazy glue to any knot or connection to the crazy circuits components. This will ensure your circuit will continue to work over time.

Step 11



• You're ready to scare!